



Digital Logic and Computer Architecture – CS322M

Satyajit Das

Assistant Professor, Dept CSE

Co-Founder – Revin Tech

satyajit.das@iitg.ac.in

What will we learn?

- **Introduction to Verilog**
- **Combinational Logic in Verilog**
- **Structural Modeling**

Hardware Description Languages

- In the beginning HDLs were developed as a 'standard way' of drawing circuit schematics.
- Modeled the interface of circuits, described how they were connected
- Allowed connections between these modules
- Supported some common logic functions
 - AND OR NOT XOR
 - Multiplexers

RESET

IC 2

IC 3

IC 4

IC 5

IC 6

IC 7

IC 8

IC 9

IC 10

IC 11

IC 12

IC 13

IC 14

IC 16

IC 17

IC 18

40077

GATE ARRAY

IC1

Z80A-CPU

DRAM 64K * 4

DRAM 64K * 4

256K - ROM

256K - ROM

DRAM 64K * 4

DRAM 64K * 4

TEA2000

MC1376

MC1488

MC1489

AY-3-8912

HCT273

765-FDC

SED9420

CENTRONICS

PERITEL RGB

CASSETTE PCB

AUDIO

DRIVE 0

DRIVE 1

JOYSTICKS

KEYBOARD - Y

RS232/MIDI

KEYPAD

NOTE: (1) *3A USE ONLY
IC10, IC20
R77, R86
C41, C47
X2
(2) *2A USE ONLY
IC100, TR100
R100, R116
C48, C100 - C111
L100, L101

(3) PERITEL ONLY VERSION
The RF output may be omitted on
Peritel only version by omitting the
following components:
IC8, IC10
TR1, TR3
C25, C31
R28, R30, R44, R46, R55, R56, R60
C22, C28, C29, C32, C33, C40, C50
L2, L3
V1 RF output antenna

ISSUE DATE
1 - 11/12/86
2 - 15/12/86
3 - 26/1/87

Convenient Way of Drawing Schematics

- It is standard
 - Everybody will interpret the schematic the same way
- It is not proprietary
 - HDLs are not tool specific
- It is machine readable
 - It is easier for computers to understand the circuit
- Only later on additional benefits were discovered
 - Simulation and Synthesis

Two Hardware Description Languages

- **Verilog**

- developed in 1984 by Gateway Design Automation
- became an IEEE standard (1364) in 1995
- More popular in US

- **VHDL (VHSIC Hardware Description Language)**

- Developed in 1981 by the Department of Defense
- Became an IEEE standard (1076) in 1987
- More popular in Europe

- In this course we will use Verilog

Defining a module

- A module is the main building block in Verilog
- We first need to declare:
 - Name of the module
 - Types of its connections (input, output)
 - Names of its connections



Defining a module

```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
  
endmodule
```



A question of style

The following two codes are identical

```
module test ( a, b, y );  
    input a;  
    input b;  
    output y;  
  
endmodule
```

```
module test ( input a,  
              input b,  
              output y );  
  
endmodule
```

What if we have busses?

- You can also define multi-bit busses.
 - [range_start : range_end]
- Example:

```
input  [31:0] a;    // a[31], a[30] .. a[0]
output [15:8] b1;   // b1[15], b1[14] .. b1[8]
output [7:0]  b2;   // b2[7], b2[6] .. b1[0]
input                clk; // single signal
```

Basic Syntax

- Verilog is case sensitive:
 - `SomeName` and `somename` are not the same!
- Names cannot start with numbers:
 - `2good` is not a valid name
- Whitespace is ignored

```
// Single line comments start with a //  
  
/* Multiline comments  
   are defined like this */
```


Good Practices

- Develop/use a consistent naming style
- Use MSB to LSB ordering for busses (little-endian)
 - Try using “a[31:0]” and not “a[0:31]”
- Define one module per file
 - Makes managing your design hierarchy easier
- Use a file name that equals module name
 - i.e. module TryThis is defined in a file called TryThis.v

There are Two Main Styles of HDL

- Structural
 - Describe how modules are interconnected
 - Each module contains other modules (instances)
 - ... and interconnections between these modules
 - Describes a hierarchy
- Behavioral
 - The module body contains functional description of the circuit
 - Contains logical and mathematical operators
- Practical circuits would use a combination of both


Structural HDL: Instantiating a Module

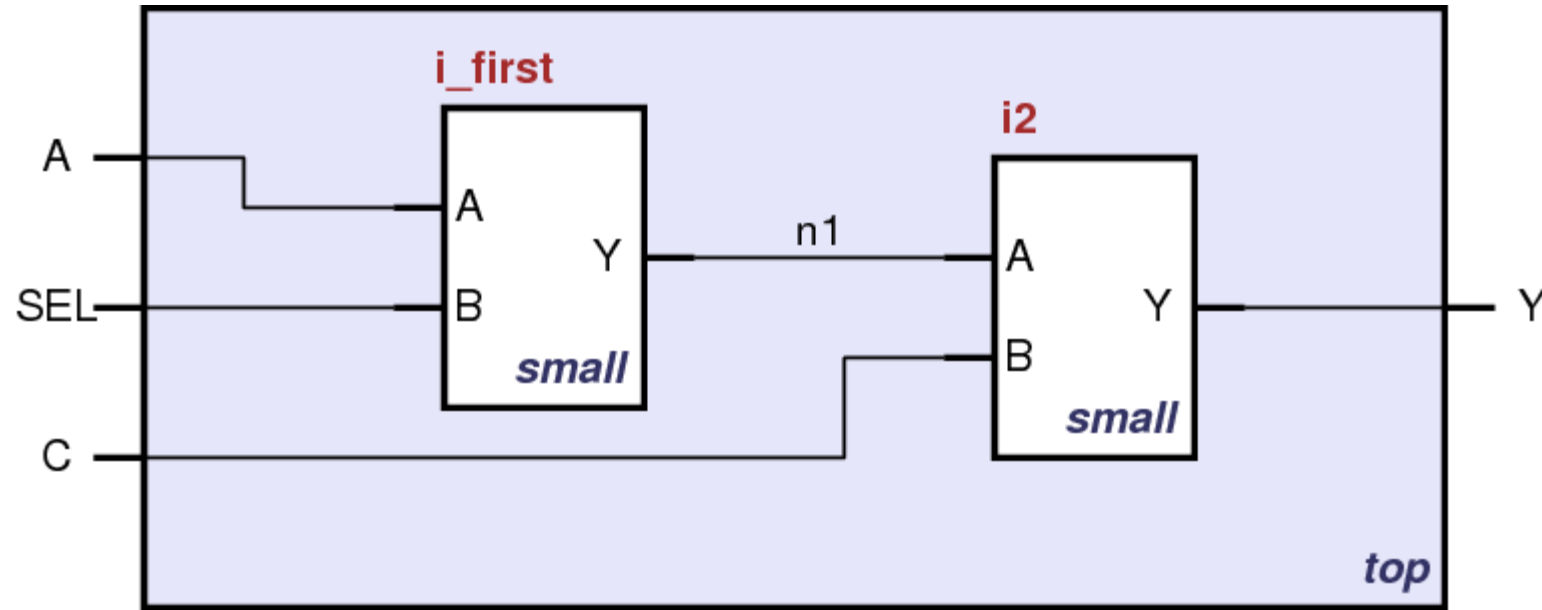

Structural HDL Example

Module Definitions

```
module top (A, SEL, C, Y);
  input A, SEL, C;
  output Y;
  wire n1;
```

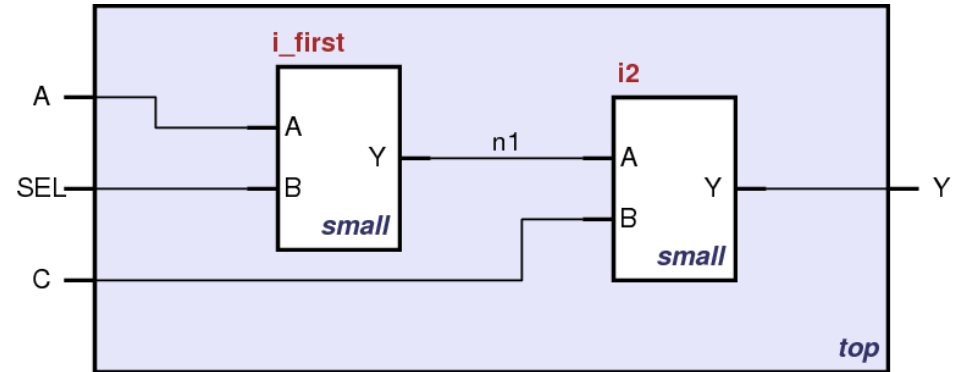endmodule


```
module small (A, B, Y);
  input A;
  input B;
  output Y;
```

```
endmodule
```

Structural HDL Example

Module Definitions
 
```
module top (A, SEL, C, Y);  
    input A, SEL, C;  
    output Y;  
    wire n1;
```




```
module small(A, B, Y);  
    input A;  
    input B;  
    output Y;  
  
    // description of small  
  
endmodule
```


Structural HDL Example

Wire definitions

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

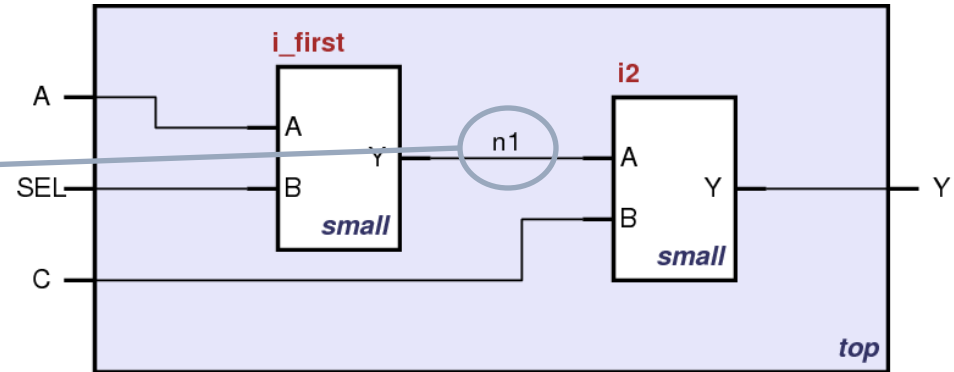

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```


```
// description of small
```

```
endmodule
```

Structural HDL Example

Instantiate first module
 
```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // instantiate small once  
  small i_first ( .A(A),  
                  .B(SEL),  
                  .Y(n1) );  
  
endmodule
```




```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

Structural HDL Example

Instantiate second module
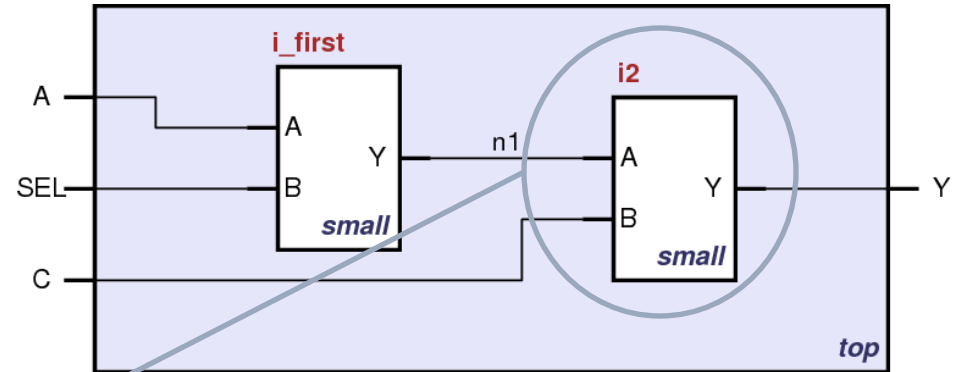
```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // instantiate small once  
  small i_first ( .A(A),  
                  .B(SEL),  
                  .Y(n1) );  
  
  // instantiate small second time  
  small i2 ( .A(n1),  
             .B(C),  
             .Y(Y) );  
  
endmodule
```




```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

Structural HDL Example

Short Instantiation
 
```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // alternative  
  small i_first ( A, SEL, n1 );  
  
  /* Shorter instantiation,  
     pin order very important */  
  
  // any pin order, safer choice  
  small i2 ( .B(C),  
             .Y(Y),  
             .A(n1) );  
  
endmodule
```



```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```


What Happens with HDL code?

- Automatic Synthesis
 - Modern tools are able to map a behavioral HDL code into gate-level schematics
 - They can perform many optimizations
 - ... however they can not guarantee that a solution is optimal
 - Most common way of Digital Design these days
- Simulation
 - Allows the behavior of the circuit to be verified without actually manufacturing the circuit
 - Simulators can work on behavioral or gate-level schematics


Behavioral HDL: Defining Functionality

```
module example (a, b, c, y);  
  
    input a;  
  
    input b;  
  
    input c;  
  
    output y;  
  
  
    // here comes the circuit description  
  
    assign y = ~a & ~b & ~c |  
               a & ~b & ~c |  
               a & ~b & c;  
  
endmodule
```

Behavioral HDL: Synthesis Results

 

Behavioral HDL: Simulating the Circuit

 

Bitwise Operators

```
module gates(input  [3:0]  a, b,  
              output [3:0] y1, y2, y3, y4, y5);
```

```
    /* Five different two-input logic
```

```
       gates acting on 4 bit busses */
```

```
    assign y1 = a & b;    // AND
```

```
    assign y2 = a | b;    // OR
```


```
    assign y3 = a ^ b;    // XOR
```

```
    assign y4 = ~(a & b); // NAND
```

```
    assign y5 = ~(a | b); // NOR
```

```
endmodule
```


Bitwise Operators: Synthesis Results

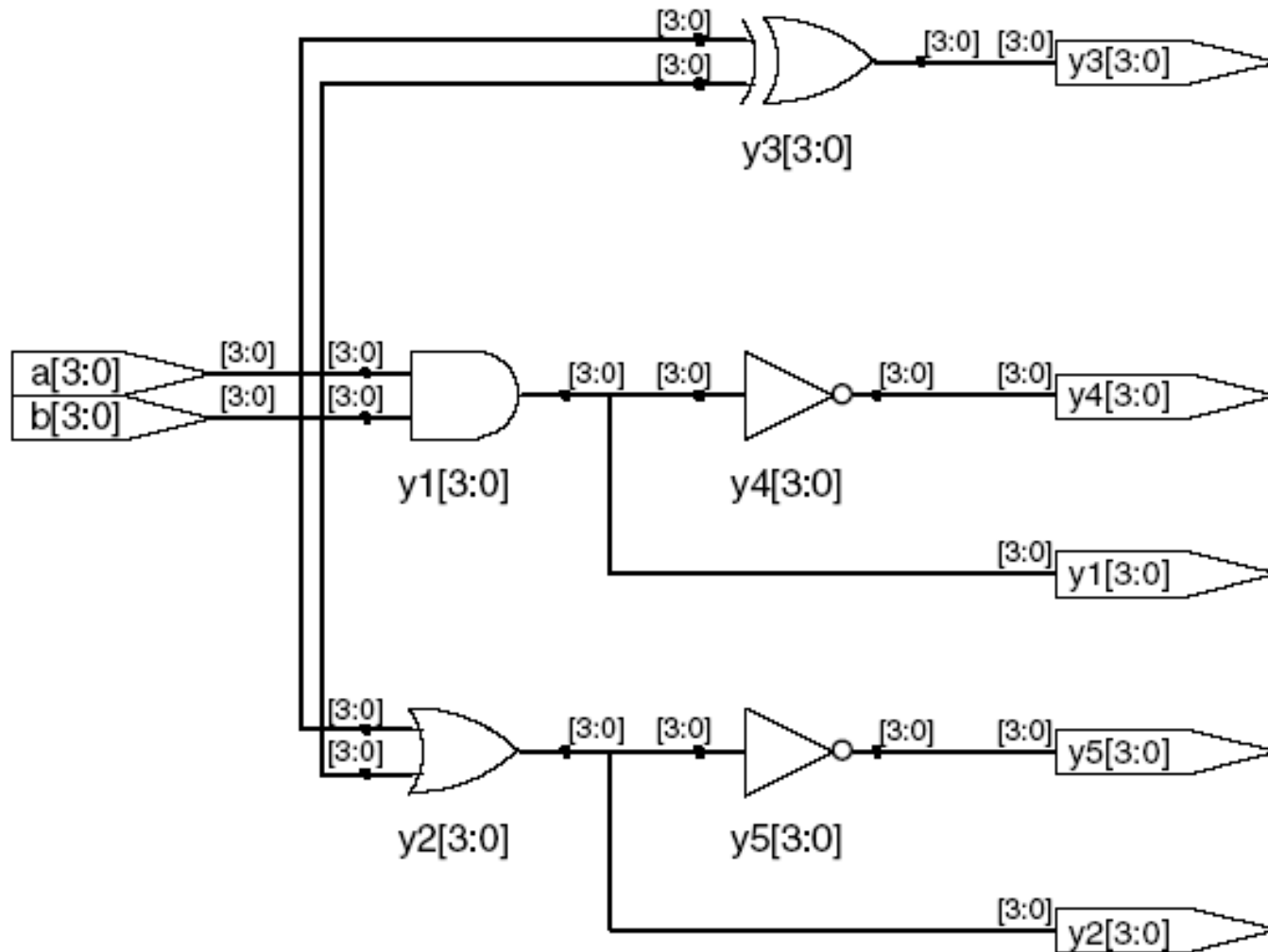

Reduction Operators

```
module and8(input  [7:0] a,  
            output      y);  
  
    assign y = &a;  
  
    // &a is much easier to write than  
    // assign y = a[7] & a[6] & a[5] & a[4] &  
    //           a[3] & a[2] & a[1] & a[0];  
  
endmodule
```

Reduction Operators: assign y = &a;

 


Conditional Assignment

```
module mux2(input [3:0] d0, d1,  
            input      s,  
            output [3:0] y);  
  
    assign y = s ? d1 : d0;  
    // if (s) then y=d1 else y=d0;  
  
endmodule
```

- ? : is also called a **ternary operator** as it operates on three inputs:
 - s
 - d1
 - d0.

 Conditional Assignment: $y = s ?$
 $d1 : d0;$



More Conditional Assignments

```
module mux4(input  [3:0] d0, d1, d2, d3
            input  [1:0] s,
            output [3:0] y);

    assign y = s[1] ? ( s[0] ? d3 : d2)
              : ( s[0] ? d1 : d0);

    // if (s1) then
    //     if (s0) then y=d3 else y=d2
    // else
    //     if (s0) then y=d1 else y=d0

endmodule
```

Even More Conditional Assignments

```
module mux4(input  [3:0] d0, d1, d2, d3
            input  [1:0] s,
            output [3:0] y);

    assign y = (s == 2'b11) ? d3 :
               (s == 2'b10) ? d2 :
               (s == 2'b01) ? d1 :
               d0;

    // if    (s = "11" ) then y= d3
    // else if (s = "10" ) then y= d2
    // else if (s = "01" ) then y= d1
    // else           y= d0

endmodule
```


How to Express numbers ?

N'Bxx

8'b0000_0001

- (N) Number of bits
 - Expresses how many bits will be used to store the value
- (B) Base
 - Can be b (binary), h (hexadecimal), d (decimal), o (octal)
- (xx) Number
 - The value expressed in base, apart from numbers it can also have X and Z as values.
 - Underscore _ can be used to improve readability

Number Representation in Verilog

Verilog	Stored Number	Verilog	Stored Number
4'b1001	1001	4'd5	0101
8'b1001	0000 1001	12'hFA3	1111 1010 0011
8'b0000_1001	0000 1001	8'o12	00 001 010
8'bx0X1zZ1	XX0X 1ZZ1	4'h7	0111
'b01	0000 .. 0001	12'h0	0000 0000 0000

What have seen so far:

- Describing structural hierarchy with Verilog
 - Instantiate modules in an other module
- Writing simple logic equations
 - We can write AND, OR, XOR etc
- Multiplexer functionality
 - If ... then ... else
- We can describe constants
- But there is more:

Precedence of operations in Verilog

Highest

~	NOT
*, /, %	mult, div, mod
+, -	add,sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
?:	ternary operator

Lowest

Example: Comparing two numbers

An XNOR gate

```
module MyXnor (input a, b,  
               output z);  
  
    assign z = ~(a ^ b); //not XOR  
  
endmodule
```

An AND gate

```
module MyAnd (input a, b,  
              output z);  
  
    assign z = a & b;    // AND  
  
endmodule
```

Example: Comparing Two Numbers

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
```

```
                output eq);
```

```
    wire c0, c1, c2, c3, c01, c23;
```

```
MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
```

```
MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
```

```
MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
```

```
MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
```

```
MyAnd haha (.A(c0), .B(c1), .Z(c01) ); // AND
```

```
MyAnd hoho (.A(c2), .B(c3), .Z(c23) ); // AND
```

```
MyAnd hihi (.A(c01), .B(c23), .Z(eq) ); // AND
```

```
endmodule
```

Example: Comparing Two Numbers

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,  
                output eq);  
    wire c0, c1, c2, c3, c01, c23;  
  
    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR  
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR  
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR  
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR  
  
    assign c01 = c0 & c1;  
    assign c23 = c2 & c3;  
    assign eq  = c01 & c23;  
  
endmodule
```

Example: Comparing Two Numbers

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,  
                output eq);  
    wire c0, c1, c2, c3;  
  
    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR  
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR  
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR  
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR  
  
    assign eq  = c0 & c1 & c2 & c3;  
  
endmodule
```


Example: Comparing Two Numbers

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,  
                output eq);
```

```
    wire [3:0] c; // bus definition
```

```
    MyXnor i0 (.A(a0), .B(b0), .Z(c[0]) ); // XNOR
```

```
    MyXnor i1 (.A(a1), .B(b1), .Z(c[1]) ); // XNOR
```

```
    MyXnor i2 (.A(a2), .B(b2), .Z(c[2]) ); // XNOR
```

```
    MyXnor i3 (.A(a3), .B(b3), .Z(c[3]) ); // XNOR
```

```
    assign eq  = &c; // short format
```

```
endmodule
```

Example: Comparing Two Numbers

```
module compare (input [3:0] a, input [3:0] b,  
                output eq);  
    wire [3:0] c; // bus definition  
  
    MyXnor i0 (.A(a[0]), .B(b[0]), .Z(c[0]) ); // XNOR  
    MyXnor i1 (.A(a[1]), .B(b[1]), .Z(c[1]) ); // XNOR  
    MyXnor i2 (.A(a[2]), .B(b[2]), .Z(c[2]) ); // XNOR  
    MyXnor i3 (.A(a[3]), .B(b[3]), .Z(c[3]) ); // XNOR  
  
    assign eq  = &c; // short format  
  
endmodule
```

Example: Comparing Two Numbers

```
module compare (input [3:0] a, input [3:0] b,  
                output eq);
```

```
    wire [3:0] c; // bus definition
```

```
    assign c = ~(a ^ b); // XNOR
```

```
    assign eq = &c; // short format
```

```
endmodule
```

Example: Comparing Two Numbers

```
module compare (input [3:0] a, input [3:0] b,  
                output eq);
```

```
assign eq = (a == b) ? 1 : 0; // really short
```

```
endmodule
```

What is the BEST way of writing Verilog

- Quite simply **IT DOES NOT EXIST!**
- Code should be easy to understand
 - Sometimes longer code is easier to comprehend
- Hierarchy is very useful
 - In the previous example it did not look like that, but for larger designs it is indispensable
- Try to stay closer to hardware
 - After all the goal is to design hardware

Parameterized Modules

```
module mux2
  #(parameter width = 8) // name and default value
  (input [width-1:0] d0, d1,
   input s,
   output [width-1:0] y);

  assign y = s ? d1 : d0;
endmodule
```

- We can pass parameters to a module

Parameterized Modules: Instantiating

```
module mux2
  #(parameter width = 8) // name and default value
  (input [width-1:0] d0, d1,
   input s,
   output [width-1:0] y);

  assign y = s ? d1 : d0;
endmodule
```


- // If parameter is not given, default is assumed (here 8)
- mux2 i_mux (d0, d1, s, out);
- // The same module with 12-bit bus width:
- mux2 #(12) i_mux_b (d0, d1, s, out);
- // More verbose version:
- mux2 #(.width(12)) i_mux_b (.d0(d0), .d1(d1),
• .s(s), .out(out));

Manipulating Bits

- `// You can assign partial busses`
- `wire [15:0] longbus;`
- `wire [7:0] shortbus;`
- `assign shortbus = longbus[12:5];`
- `// Concatenating is by {}`
- `assign y = {a[2],a[1],a[0],a[0]};`
- `// Possible to define multiple copies`
- `assign x = {a[0], a[0], a[0], a[0]}`
- `assign y = { 4{a[0]} }`

Z floating output
 
```
module tristate(input  [3:0] a,  
                input    en,  
                output [3:0] y);  
  
    assign y = en ? a : 4'bz;  
  
endmodule
```



Truth Table for AND with Z and X

&		A			
		0	1	Z	X
B	0	0	0	0	0
	1	0	1	X	X
	Z	0	X	X	X
	X	0	X	X	X

What About Timing ?

- It is possible to define timing relations in Verilog
 - These are **ONLY** for Simulation
 - They **CAN NOT** be synthesized
 - They are used for modeling delays in simulation


```
'timescale 1ns/1ps
module simple (input a, output z1, z2);

  assign #5 z1 = ~a; // inverted output after 5ns
  assign #9 z2 = a;  // output after 9ns

endmodule
```

 Tasks to do

- **L1.1. Design a 1-bit comparator circuit that has two 1-bit binary inputs (A and B) and outputs a logic-1 on first output port (o1) if $A > B$, and outputs logic-1 on second output port (o2) if $A = B$, and outputs logic-1 on the third output port (o3) if $A < B$.**
- L1.2. Design a 4-bit equality comparator circuit that has two 4-bit binary inputs (A and B) and outputs a logic-1 if both inputs are equal.



Next Steps

- We have seen an overview of Verilog
- Discussed behavioral and structural modeling
- Showed combinational logic constructs

Still to come: (later)

- Sequential circuit description in Verilog
- Developing testbenches for simulation