



Digital Logic and Computer Architecture – CS322M

Satyajit Das

Assistant Professor, Dept CSE

Co-Founder – Revin Tech

satyajit.das@iitg.ac.in

What will we learn?


- **Timing of Sequential Logic**
 - Setup time
 - Hold time
- **Clock frequency**
- **Metastability and prevention**

Timing

- Flip-flop samples D at clock edge
- D must be stable when it is sampled
- Similar to a photograph, D must be stable around the clock edge
- If D is changing when it is sampled, *metastability* can occur
 - Recall that a flip-flop copies the input D to the output Q on the rising edge of the clock. This process is called sampling D on the clock edge. If D is stable at either 0 or 1 when the clock rises, this behavior is clearly defined. But what happens if D is changing at the same time the clock rises?


Input Timing Constraints

 - **Setup time:** t_{setup} = time before the clock edge that data must be stable (i.e. not changing)
- **Hold time:** t_{hold} = time after the clock edge that data must be stable
- **Aperture time:** t_a = time around clock edge that data must be stable ($t_a = t_{\text{setup}} + t_{\text{hold}}$)




Output Timing Constraints

 - **Propagation delay:** t_{pcq} = time after clock edge that the output Q is guaranteed to be stable (i.e., to stop changing)
- **Contamination delay:** t_{ccq} = time after clock edge that Q might be unstable (i.e., start changing)




Dynamic Discipline

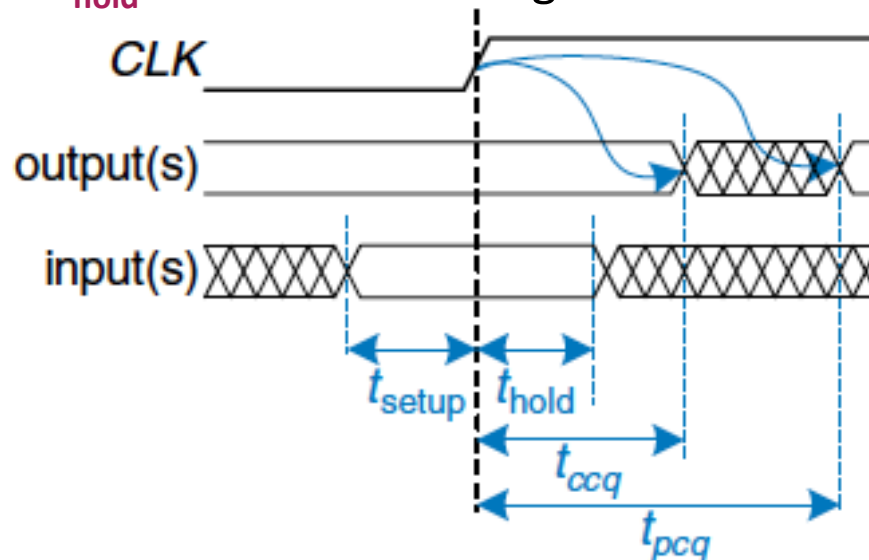- The input to a synchronous sequential circuit must be stable during the aperture (setup and hold) time around the clock edge.
- Specifically, the input must be stable
 - at least t_{setup} before the clock edge
 - at least until t_{hold} after the clock edge



Dynamic Discipline

 - The delay between registers has a minimum and maximum delay, dependent on the delays of the circuit elements




Setup Time Constraint

- The clock period or cycle time, T_c , is the time between rising edges of a repetitive clock signal. Its reciprocal, $f_c=1/T_c$, is the clock frequency.
- All else being the same, increasing the clock frequency increases the work that a digital system can accomplish per unit time.
- Frequency is measured in units of Hertz (Hz), or cycles per second:
 - 1 megahertz (MHz) 10^6 Hz
 - 1 gigahertz (GHz) 10^9 Hz.

Setup Time Constraint

 
- The setup time constraint depends on the maximum delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least t_{setup} before the clock edge.



$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$

Setup Time Constraint

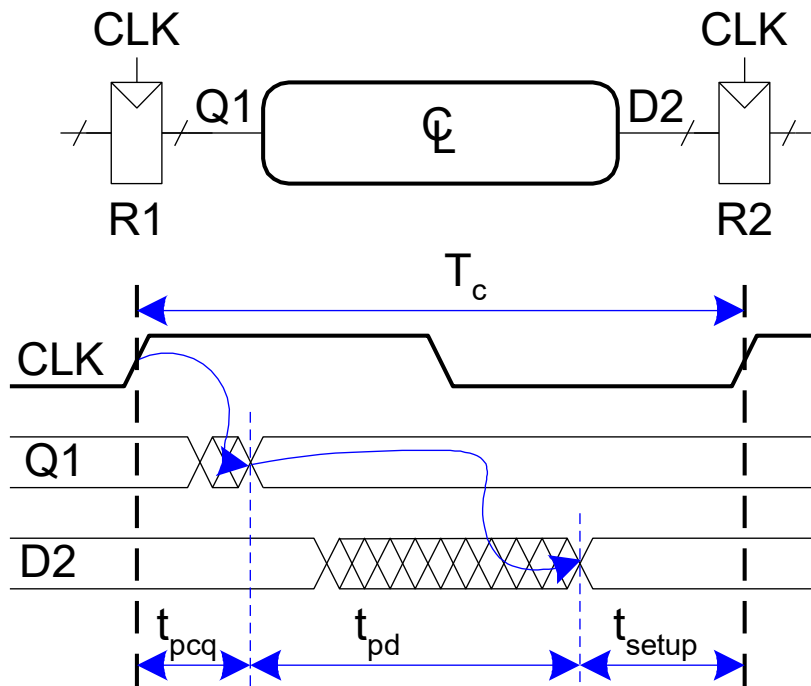- The setup time constraint depends on the maximum delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least t_{setup} before the clock edge.




$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$

$$t_{pd} \leq$$

Setup Time Constraint

 - The setup time constraint depends on the maximum delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least t_{setup} before the clock edge.




$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$

$$t_{pd} \leq T_c - (t_{pcq} + t_{\text{setup}})$$

Hold Time Constraint

 
- The hold time constraint depends on the minimum delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least t_{hold} after the clock edge.



$t_{\text{hold}} <$

Hold Time Constraint

 
- The hold time constraint depends on the minimum delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least t_{hold} after the clock edge.



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$
$$t_{\text{cd}} >$$


Hold Time Constraint

 - The hold time constraint depends on the minimum delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least t_{hold} after the clock edge.



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$
$$t_{\text{cd}} > t_{\text{hold}} - t_{\text{ccq}}$$

Timing Analysis

 

$$t_{pd} =$$

$$t_{cd} =$$

Setup time constraint:

$$T_c \geq$$

$$f_c = 1/T_c =$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$


per gate

$$\left[\begin{array}{ll} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{array} \right.$$

Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

Timing Analysis

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$\text{per gate} \left[\begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$


Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

$$(30 + 25) \text{ ps} > 70 \text{ ps} ? \text{ No!}$$

Fixing Hold Time Violation

Add buffers to the short paths:

 

$$t_{pd} =$$

$$t_{cd} =$$

Setup time constraint:

$$T_c \geq$$

$$f_c =$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$


$$\text{per gate} \begin{cases} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{cases}$$

Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

Fixing Hold Time Violation

Add buffers to the short paths:

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$\text{per gate} \begin{cases} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{cases}$$


Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

$$(30 + 50) \text{ ps} > 70 \text{ ps} ? \text{ Yes!}$$


Clock Skew

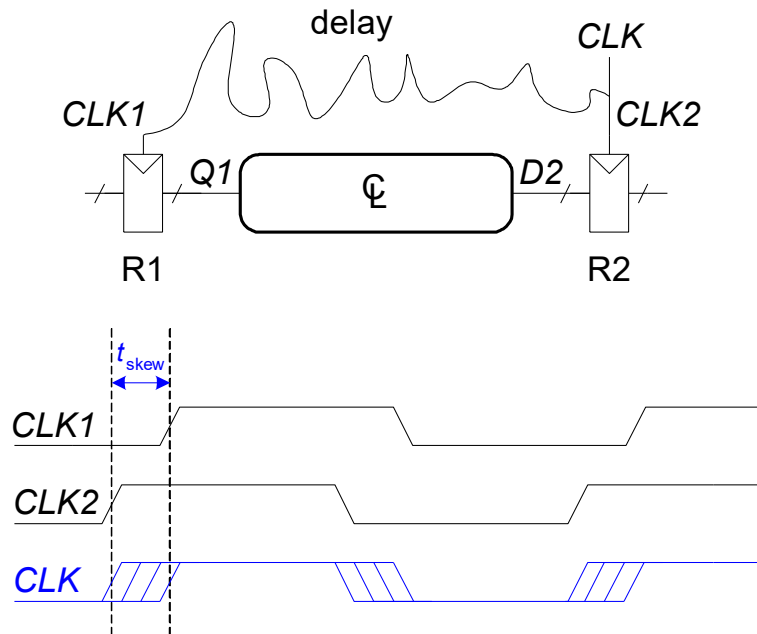- The clock doesn't arrive at all registers at the same time
- Skew is the difference between two clock edges
- Examine the worst case to guarantee that the dynamic discipline is not violated for any register – many registers in a system!




Setup Time Constraint with Clock Skew

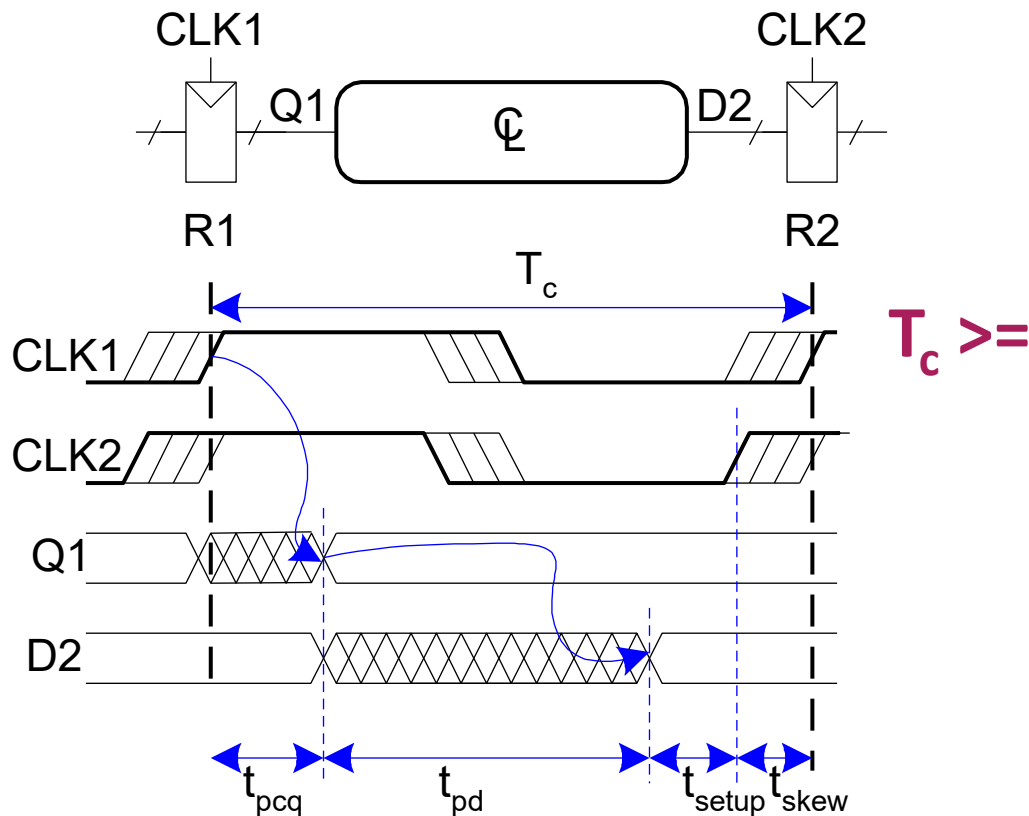- In the worst case, the CLK2 is **earlier** than CLK1



Setup Time Constraint with Clock Skew

 - In the worst case, the CLK2 is **earlier** than CLK1




$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$

$$t_{pd} \leq$$

Setup Time Constraint with Clock Skew

 - In the worst case, the CLK2 is **earlier** than CLK1




$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$

$$t_{pd} \leq T_c - (t_{pcq} + t_{setup} + t_{skew})$$

Hold Time Constraint with Clock Skew

 
- In the worst case, CLK2 is **later** than CLK1



$$t_{hold} + t_{skew} = <$$

Hold Time Constraint with Clock Skew

 - In the worst case, CLK2 is **later** than CLK1




$$t_{hold} + t_{skew} \leq t_{ccq} + t_{cd}$$

$$t_{cd} \geq$$

Hold Time Constraint with Clock Skew

 - In the worst case, CLK2 is **later** than CLK1





$$t_{hold} + t_{skew} \leq t_{ccq} + t_{cd}$$

$$t_{cd} \geq t_{hold} + t_{skew} - t_{ccq}$$


Violating the Dynamic Discipline

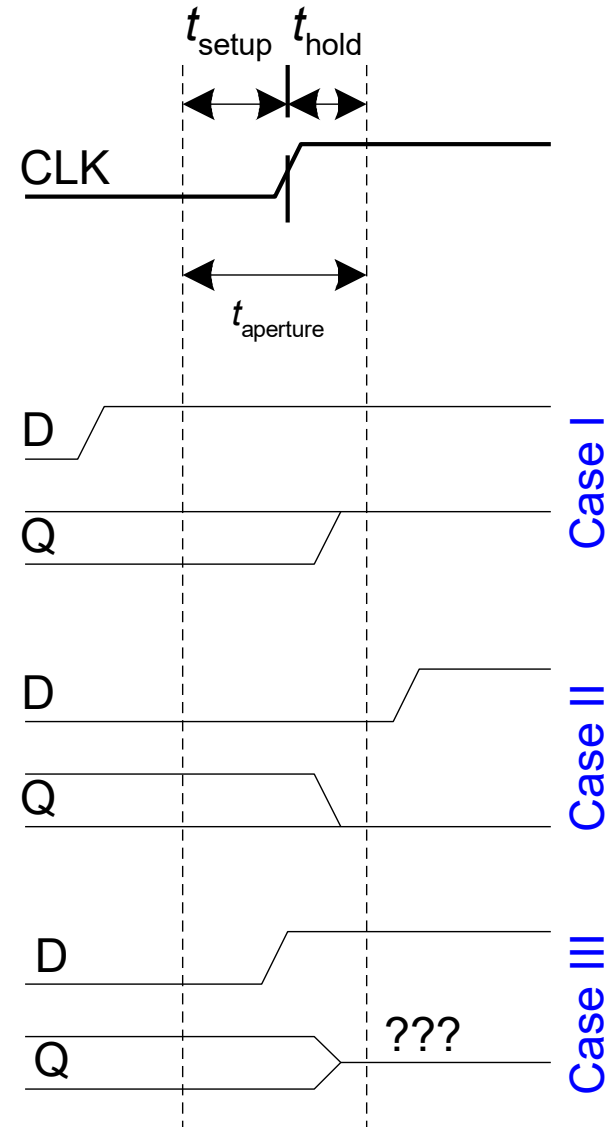 - Asynchronous (for example, user) inputs might violate the dynamic discipline



Metastability

 - Any bi-stable device has two stable states and a metastable state between them
- A flip-flop has two stable states (1 and 0) and one metastable state
- If a flip-flop lands in the metastable state, it could stay there for an undetermined amount of time



Metastability


- T_0/T_c describes the probability that the input changes at a bad time, i.e., during the aperture time

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$

- τ is a time constant indicating how fast the flip-flop moves away from the metastable state; it is related to the delay through the cross-coupled gates in the flip-flop
- In short, if a flip-flop samples a metastable input, if you wait long enough (t), the output will have resolved to 1 or 0 with high probability.


Synchronizers

 - Asynchronous inputs (D) are inevitable (user interfaces, systems with different clocks interacting, etc.).
- The goal of a synchronizer is to make the probability of failure (the output Q still being metastable) low.
- A synchronizer cannot make the probability of failure 0.



Synchronizer Internals

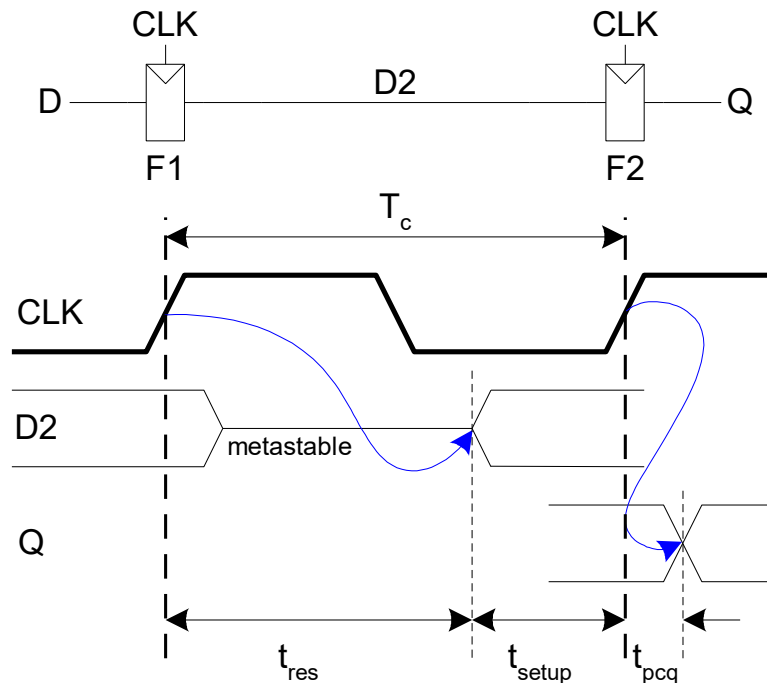
- A synchronizer can be built with two back-to-back flip-flops.
- Suppose the input D is changing when it is sampled by F1.
- Internal signal D2 has $(T_c - t_{\text{setup}})$ time to resolve a 1 or 0.



Synchronizer Probability of Failure

- For each sample, the probability of failure of this synchronizer is:
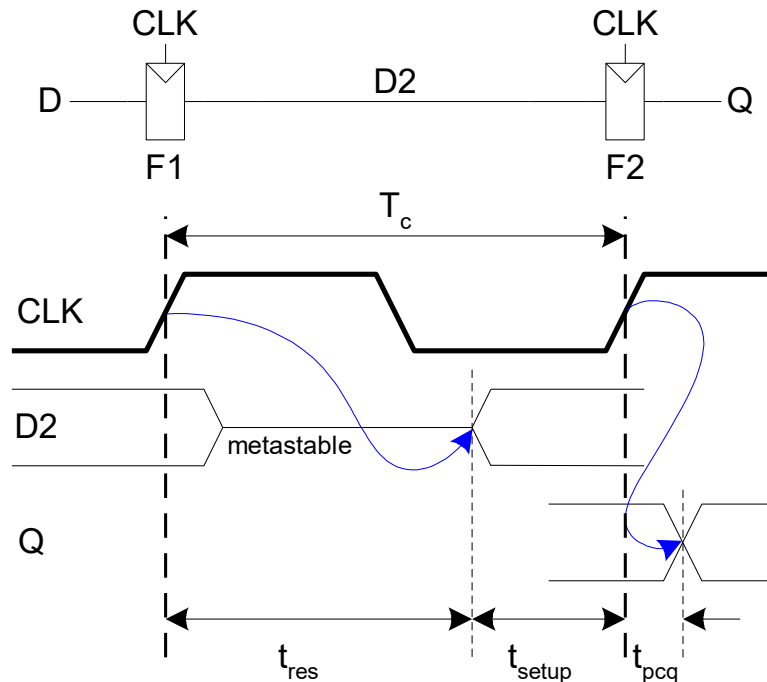
$$P(\text{failure}) = \frac{T_0}{T_c} e^{-\frac{T_c - t_{\text{setup}}}{\tau}}$$



Synchronizer Mean Time Before Failure


- If the asynchronous input changes once per second, the probability of failure per second of the synchronizer is simply $P(\text{failure})$.
- In general, if the input changes N times per second, the probability of failure per second of the synchronizer is:

$$P(\text{failure})/\text{sec} = N \frac{T_0}{T_c} e^{-\frac{T_c - t_{\text{setup}}}{\tau}}$$

- Thus, the synchronizer fails, on average, $1/[P(\text{failure})/\text{second}]$
This is called the mean time between failures, MTBF:

$$MTBF = \frac{1}{P(\text{failure})/\text{sec}} = \frac{T_c e^{\frac{T_c - t_{\text{setup}}}{\tau}}}{NT_0}$$

Example Synchronizer

 

Suppose: $T_c = 1/500 \text{ MHz} = 2 \text{ ns}$

$T_0 = 150 \text{ ps}$

$N = 10 \text{ events per second}$

$\tau = 200 \text{ ps}$

$t_{\text{setup}} = 100 \text{ ps}$

What is the probability of failure? MTBF?

$P(\text{failure}) =$


$=$

$P(\text{failure})/\text{second} =$

$=$

MTBF $=$

Example Synchronizer

 

Suppose: $T_c = 1/500 \text{ MHz} = 2 \text{ ns}$ $\tau = 200 \text{ ps}$
 $T_0 = 150 \text{ ps}$ $t_{\text{setup}} = 100 \text{ ps}$
 $N = 10 \text{ events per second}$

What is the probability of failure? MTBF?

$$P(\text{failure}) = (150 \text{ ps} / 2 \text{ ns}) e^{-(1.9 \text{ ns}) / 200 \text{ ps}}$$

$$= 5.6 \times 10^{-6}$$

$$P(\text{failure})/\text{second} = 10 \times (5.6 \times 10^{-6})$$

$$= 5.6 \times 10^{-5} / \text{second}$$

$$\text{MTBF} = 1/[P(\text{failure})/\text{second}] \approx 5 \text{ hours}$$

What did we learn ?

- **Timing constraints for sequential circuits**
 - *Setup time*, time needed for the inputs to be present before clock
 - *Hold time*, time needed after the clock where inputs should not change
 - *Aperture time*, time around clock event where inputs should stay stable
- **Problems related to clock skew**
- **Metastability and Synchronization**